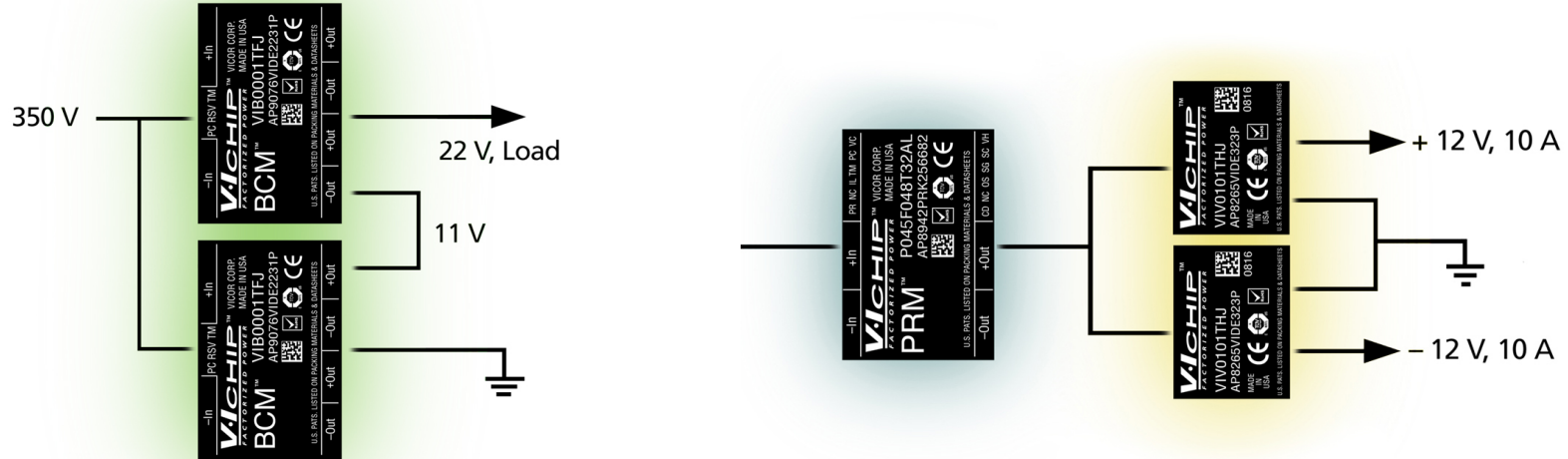


Stacked & Negative Polarity Outputs



- Mix and match BCM or VTM outputs to obtain voltages
- Can be used in series
- Isolation provides choice of output polarity